

Name: Mukund P Nuyula

USN: 1MS18CS077

Lab 5

Steps in designing ALU

Step 1: Add ² input pins

Drop two East-facing input pins on the canvas 4 bits each. Label A and B, and ensure that each input is 4 bits.

Step 2: Add the Adder/Subtractor and Guts

Now we add the subcircuits created earlier. Select the circuits under the main project folder.

Step 3: Add the multiplexers.

These take on 0 or more data inputs and generate a single output. In Logisim, multiplexers are under the plexers folder. Click the multiplex icon and drop two of them into canvas.

Step 4: Add controls

Drop two pins on the canvas north-facing with 1 data bit. Label them 0 and 1 respectively.

Step 5: Add a splitter.

Next, we add a splitter into our circuit that takes one line from the second multiplexer and splits it to 4 inputs to an OR gate - for a 4 bit ALU.

Step 6: Add another OR gate and a NOT gate

Now we add an OR gate after the splitter, which has 4 inputs. To the right of the OR gate, add a NOT gate.


This arrangement accounts for zero output when all of the bits result in zero. The NOT gate following the OR gate achieves this.

Finally, add a single bit pin after NOT gate to store the result, Label it zero


Step 7: Add a result pin for the MUX

We handled the zeroes coming from MUX, but we also need to account for valid combination inputs from A, B and the Control Inputs

1 BIT ALU (1 of 1)

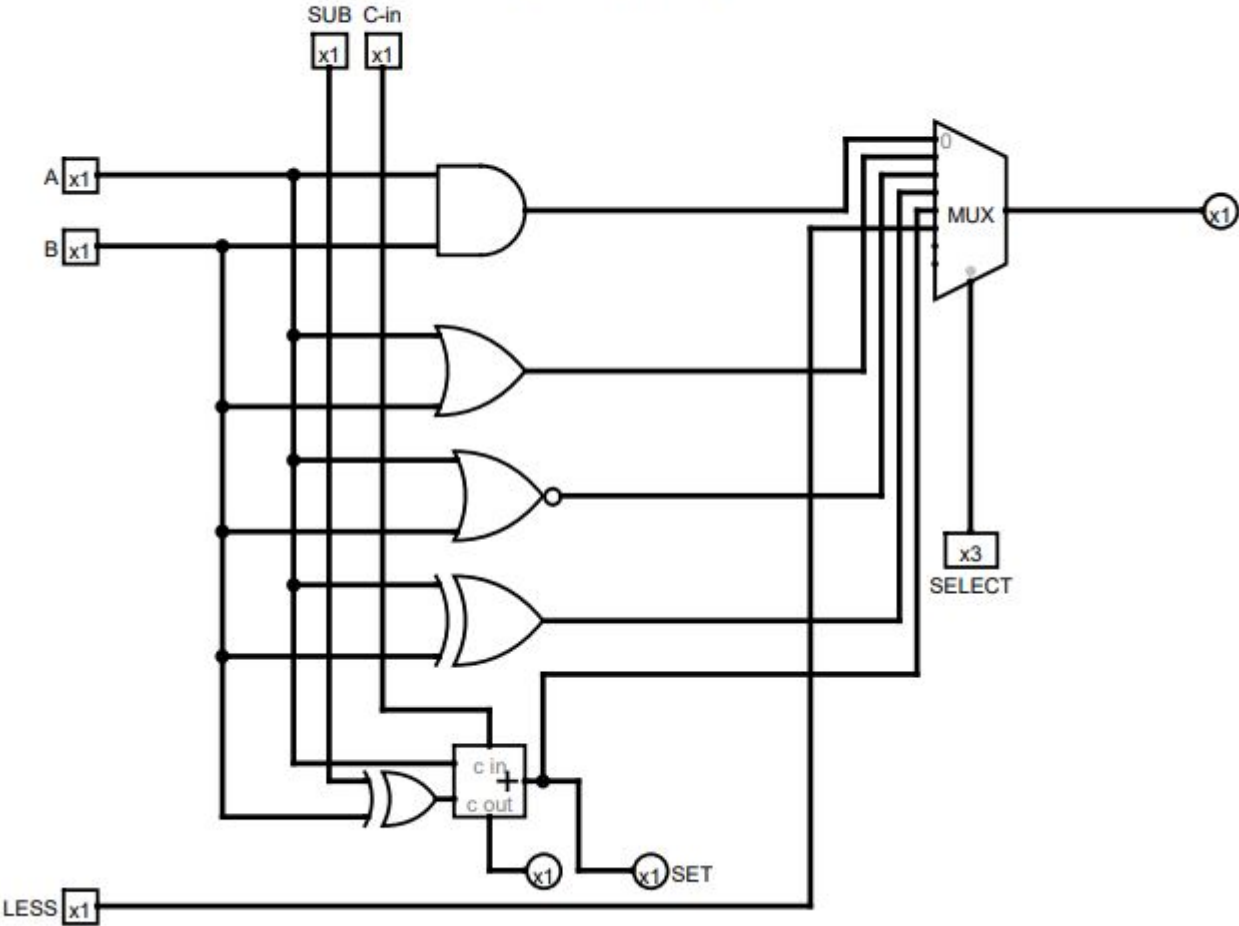

8 BIT ALU (1 of 1)

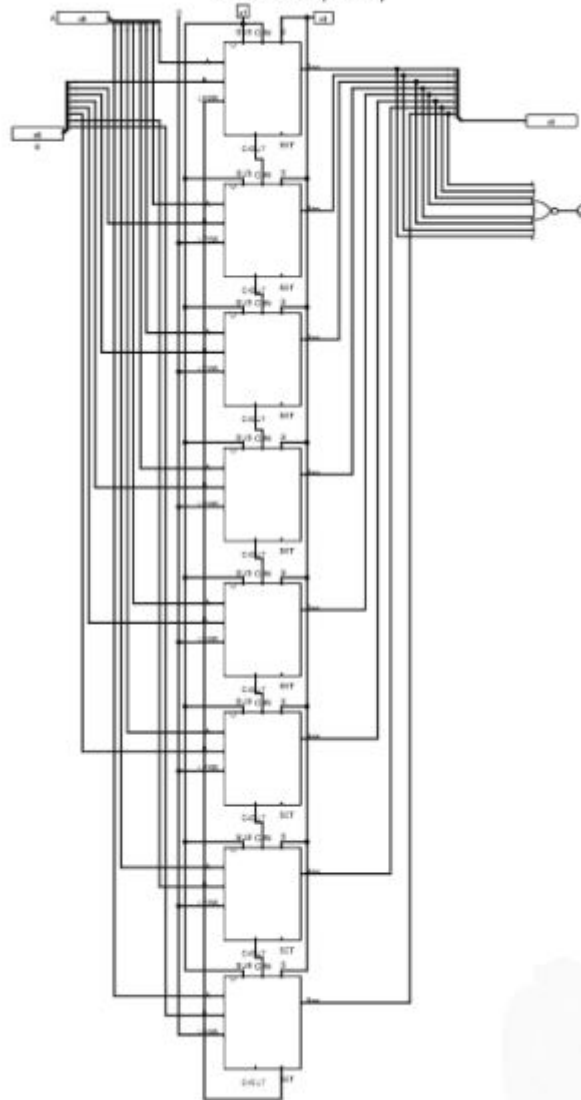

Name: Mukund P Nayak

USN: 1MS18CS077

Lab 6

Step 1: Add RAM

Select a separate load and store operation for RAM

Step 2: Add Counter

Connect Counter, Clock and Controlled Buffer to the RAM

Step 3: Add TTY

To display the data.

Step 4: Add Random Generator

To generate different address location. Add input and another Controlled Buffer to the Random Generator.

Step 5: Add Button

Connect Button to Counter.



- J-K Flip-Flop
- S-R Flip-Flop
- Register
- Counter
- Shift Register
- Random Generator
- RAM
- ROM
- Input/Output
 - Button
 - Joystick
 - Keyboard
 - LED
 - 7-Segment Display
 - Hex Digit Display
 - LED Matrix
 - TTY
- Base

Pin

Facing	North
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Location	West
Label Font	SansSerif Plain 12

100%

