

Ramaiah Institute of Technology
(Autonomous Institute, Affiliated to VTU)

Department of CSE

Programme: B.E
Course: Computer Organization

Term: Jan to May 2019
Course Code: CS45

Activity V: Designing an ALU to perform arithmetic and logical functions using Logisim simulator.

Name: Mayank Sharma	Marks: /10	Date: 22 May 2020
USN: 1MS18CS070	Signature of the Faculty:	

Objective: To simulate the working of Arithmetic and Logical Unit using simulator.



Simulator Description: Logisim is an educational tool for designing and simulating digital logic circuits. With its simple toolbar interface and simulation of circuits as you build them, it is simple enough to facilitate learning the most basic concepts related to logic circuits. With the capacity to build larger circuits from smaller sub circuits, and to draw bundles of wires with a single mouse drag, Logisim can be used (and is used) to design and simulate entire CPUs for educational purposes.

Activity to be performed by students:

List out the steps in designing ALU


- 1> Add the two i/p pins. Name them A and B
- 2> Add or, and, ex-or, nor gates and a 1-bit adder
- 3> Connect the A's and B's of all the gates to their respective pins.
- 4> Add an output pin and name it Result
- 5> Add a 1-bit multiplexer with 3 select bits
- 6> Connect outputs of all gates to the mux
- 7> Connect 3 bit input pin to mux.
- 8> Add i/p pin to cin, and output pin to Cout.
- 9> Add an ex-or gate connect its o/p to Cout. The first i/p must be connected to B and the second to another i/p pin 80B.
- 10> Add another i/p and name it left. Connect it to mux
- 11> Add an output pin and name it Set, connect it to the multiplexer output of adder unit.

Snapshots:

 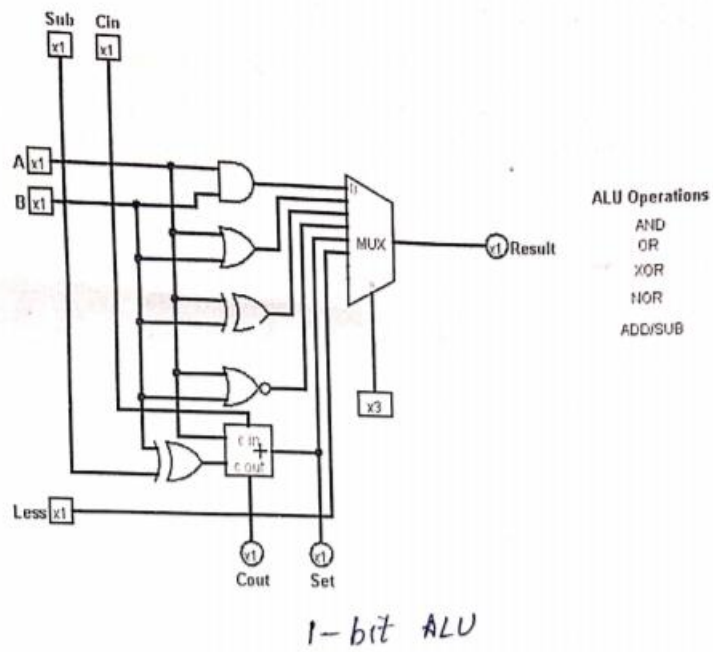

ALU object

Snapshots

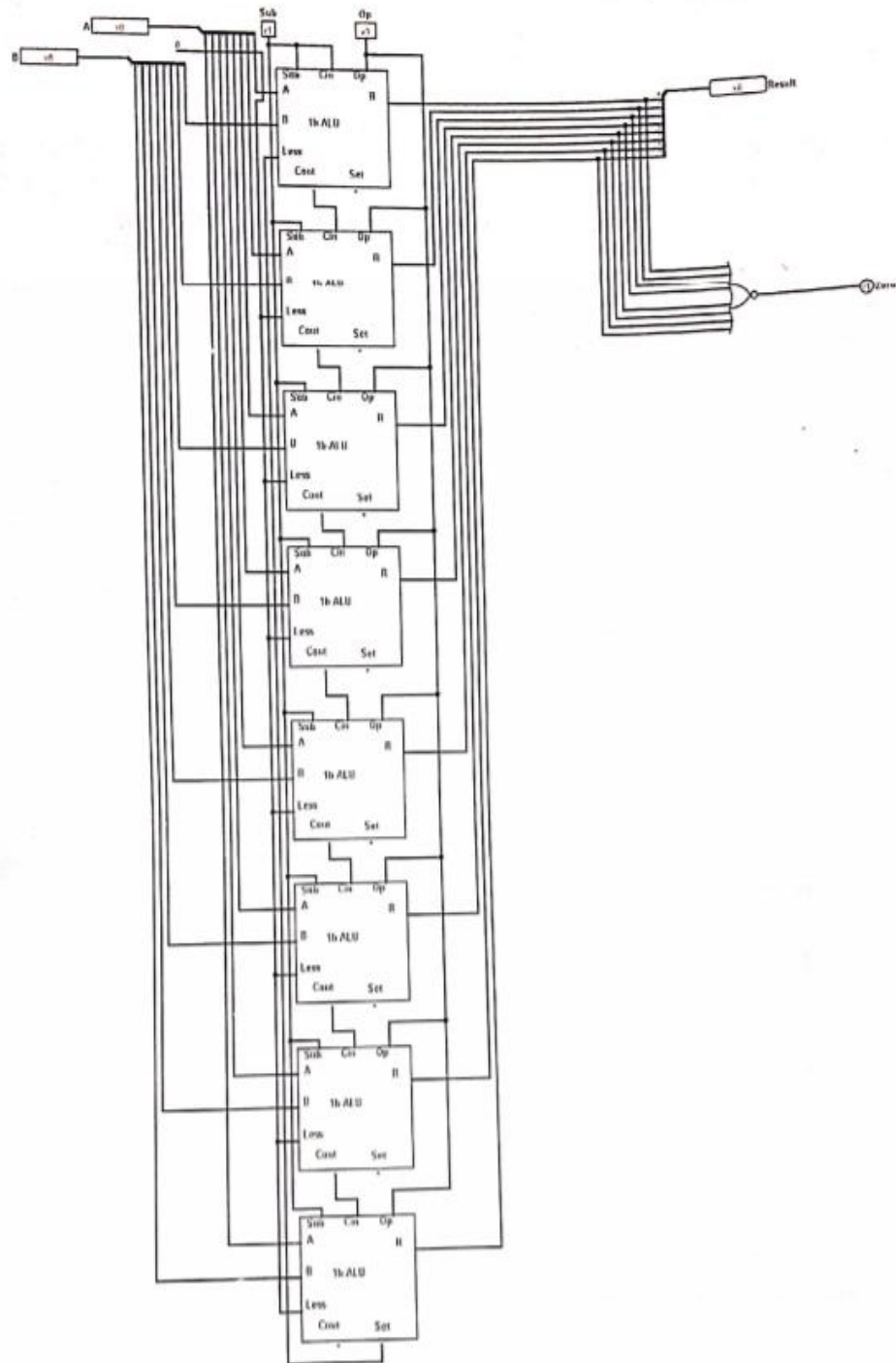

Ramaiah Institute of Technology
(Autonomous Institute, Affiliated to VTU)

Department of CSE

Programme: B.E
Course: Computer Organization

Term: Jan to May 2019
Course Code: CS45

Activity VI: Designing memory system using Logisim simulator.

Name: Mayank Sharma	Marks: /10	Date: 20 May 2020
USN: 1MS18CS070	Signature of the Faculty:	

Objective: To simulate the writing operation on memory.

Simulator Description: Logisim is an educational tool for designing and simulating digital logic circuits. With its simple toolbar interface and simulation of circuits as you build them, it is simple enough to facilitate learning the most basic concepts related to logic circuits. With the capacity to build larger circuits from smaller sub circuits, and to draw bundles of wires with a single mouse drag, Logisim can be used (and is used) to design and simulate entire CPUs for educational purposes.



Activity to be performed by students:

List out the steps in designing memory system

- 1-> Add a RAM with separate load and store selected
- 2-> Add a counter and connect 0 to A of the Ram.
- 3-> Add a Controller buffer and convert its o/p to RAM.
- 4-> Add a clock and connect to the i/p of the buffer
- 5-> Add a TTY with unit with 32 rows and columns.
Make the connections with RAM.
- 6-> Add a 7-bit random number generator, connect 0 to 0
- 7-> Add another controlled buffer connect p+ to TTY. Also add an i/p pin to the buffer.
- 8-> Connect the o/p of the second buffer to the counter.
- 9-> Connect a button to the counter.

Observations and Snapshots:

Snapshots -

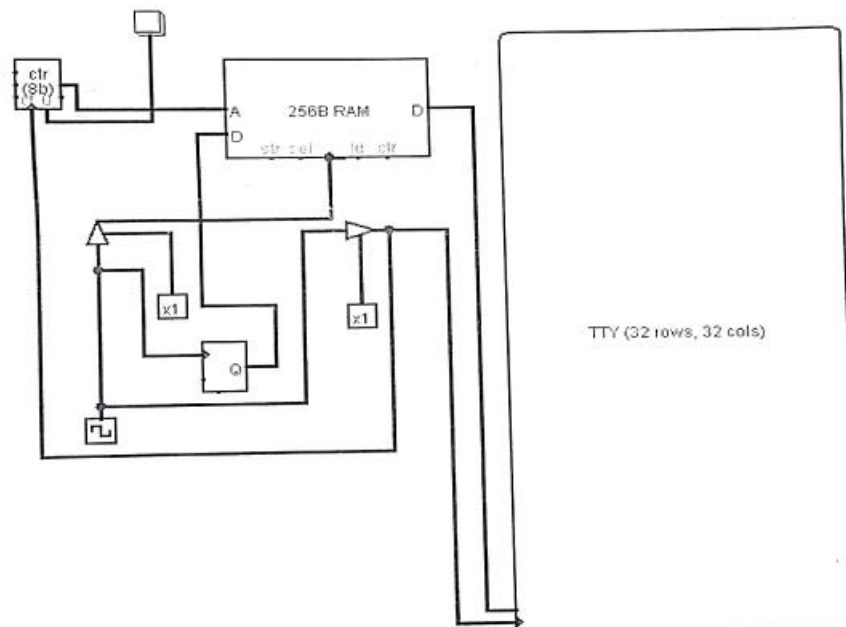 

Ramaiah Institute of Technology
(Autonomous Institute, Affiliated to VTU)

Department of CSE

Programme: B.E
Course: Computer Organization

Term: Jan to May 2019
Course Code: CS45

Activity VII: To simulate advantages of using pipeline technique in executing a program.

Name: Mayank Sharma	Marks: /10	Date: 22 May 2020
USN: 1MS18CS070	Signature of the Faculty:	

Objective: To learn and analyze the performance of the CPU by overlapping of instructions using CPUOS-SIM simulator.

Simulator Used: CPUOS-SIM is a software development environment for the simulation of simple computers. It was developed by Dale Skrien to help users to understand computer architectures.

Modern CPU's contain several semi-independent circuits involved in decoding and executing each machine instruction. Separate circuit elements perform each of these typical steps:


- Fetch the next instruction from memory into an internal CPU register.
- Decode the instruction to determine which function sub-circuits it requires.
- Read any input operands required from high-speed registers or directly from memory.
- Execute the operation using the selected sub-circuits.
- Write any output results to high-speed registers or directly to memory.

Separate sections of the CPU circuitry are used for each of these steps. This allows these circuit sections to be arranged into a sequential pipeline, with the output of one step feeding into the next step.


Activity to be performed by students:

With diagram demonstrate the execution of the following instructions using pipelining technique.

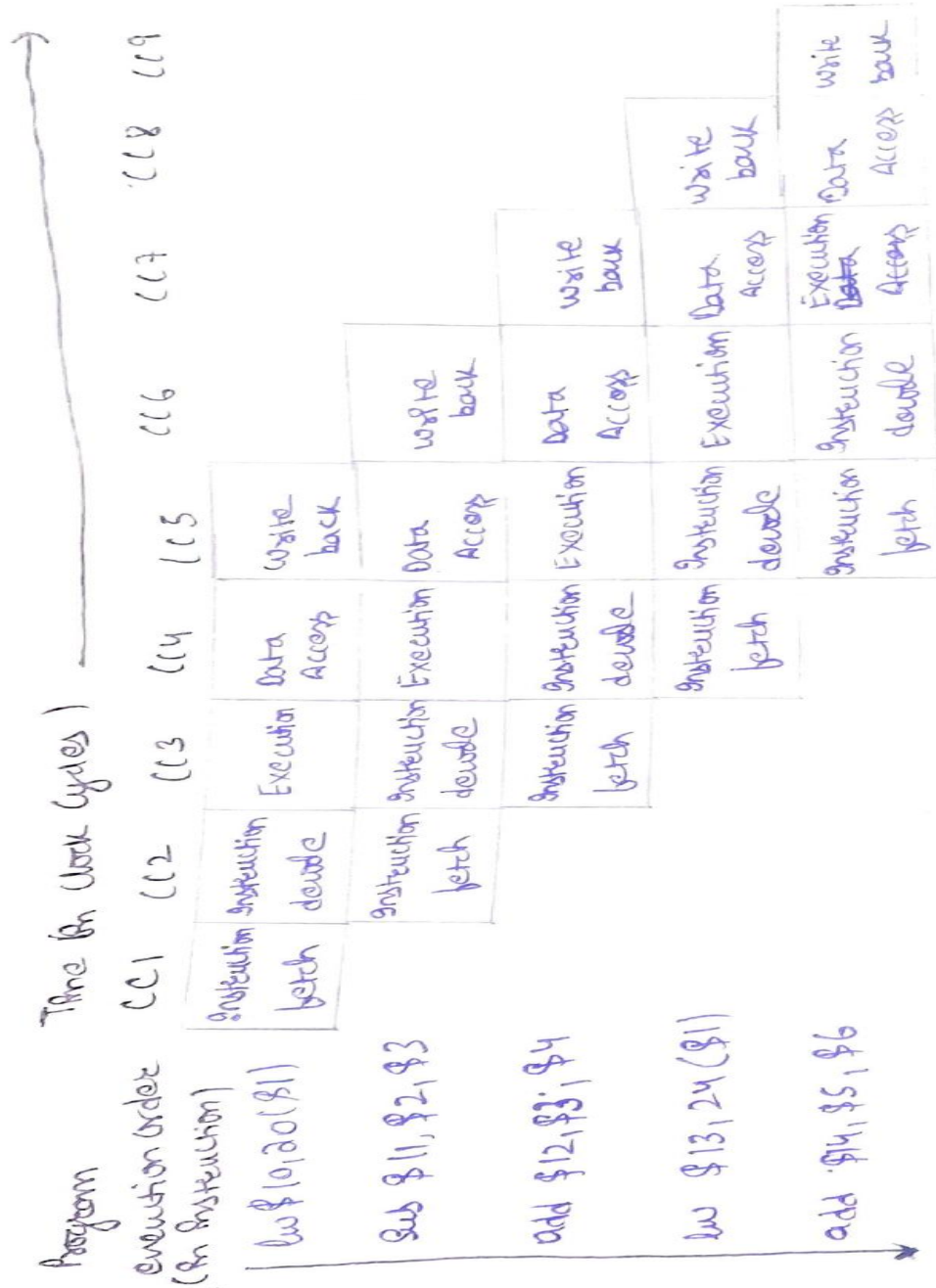lw \$10,20(\$1)
sub \$11, \$2, \$3
add \$12, \$3, \$4
lw \$13, 24(\$1)
add \$14, \$5, \$6



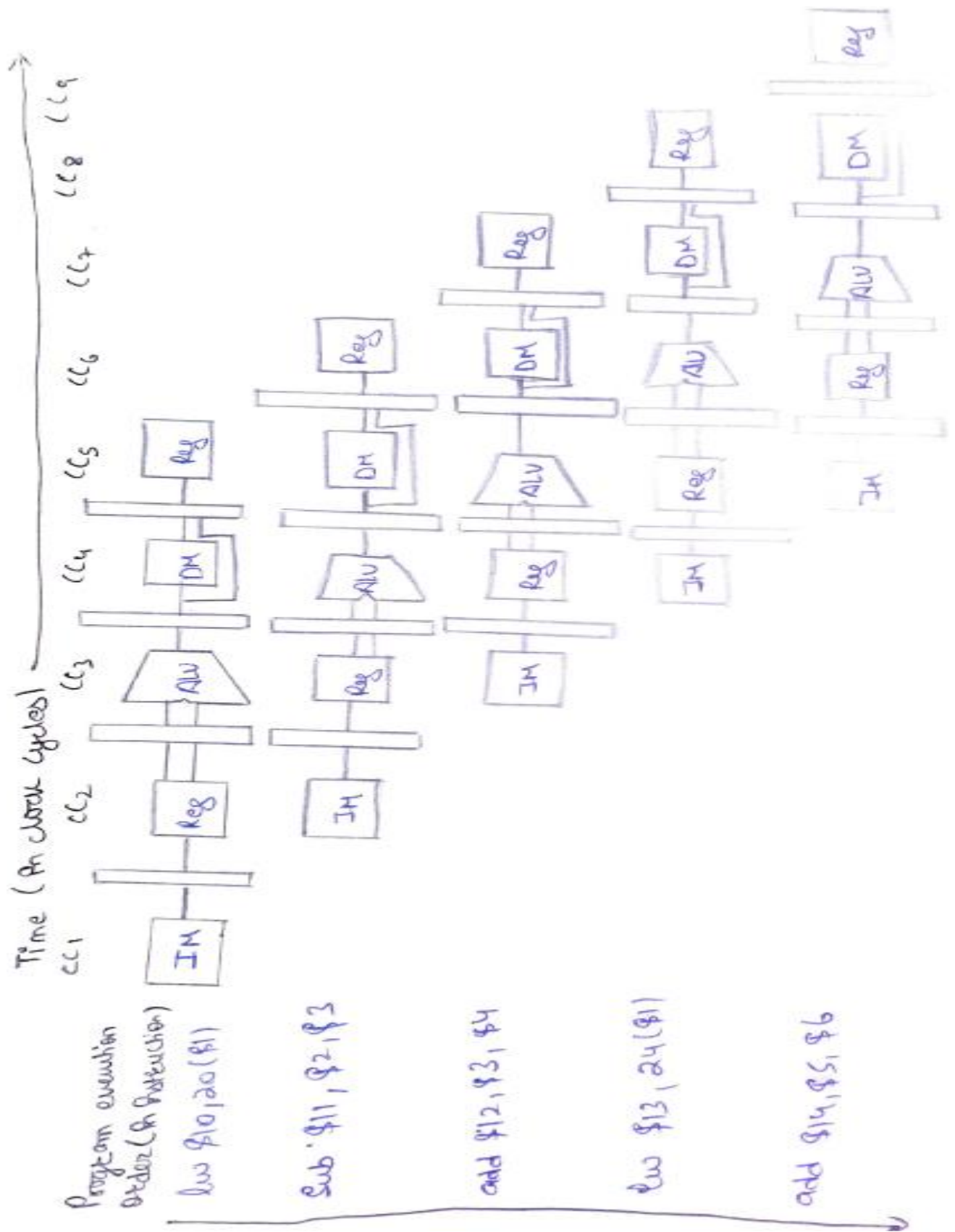Observations and Snapshots: Take the snap shot of CPU statistics and pipeline design.



Snapshots

