

Ramaiah Institute of Technology
(Autonomous Institute, Affiliated to VTU)

Department of CSE

Programme: B.E
Course: Computer Organization

Term: Jan to May 2019
Course Code: CS45

Activity V: Designing an ALU to perform arithmetic and logical functions using Logisim simulator.

Name: MUSKAN GUPTA	Marks: /10	Date: 21/5/20
USN: 1MS18CS078	Signature of the Faculty:	

Objective: To simulate the working of Arithmetic and Logical Unit using simulator.


Simulator Description: Logisim is an educational tool for designing and simulating digital logic circuits. With its simple toolbar interface and simulation of circuits as you build them, it is simple enough to facilitate learning the most basic concepts related to logic circuits. With the capacity to build larger circuits from smaller sub circuits, and to draw bundles of wires with a single mouse drag, Logisim can be used (and is used) to design and simulate entire CPUs for educational purposes.

Activity to be performed by students:


List out the steps in designing ALU

1. Add the two i/p pins, Name them A and B.
2. Add OR, AND, EX-OR, NOR gates and a 1-bit adder.
3. Connect the A's and B's of all the gates to their respective pins.
4. Add an output pin and name it Result.
5. Add a 1-bit multiplexer with 3 select bits.
6. ~~Connect~~ Connect the outputs of all gates to the mux.
7. Connect 3-bit input pin to mux.
8. Add i/p pin to Cin and output pin to Cout.
9. Add an EX-OR gate. Connect its o/p to Cout.
The first i/p must be connected to B and the second to another i/p pin SUB.
10. Add another i/p and name it Less. Connect it to mux.
11. Add an output pin and name it Set. Connect it to the multiplexer o/p of adder unit.

Snapshots

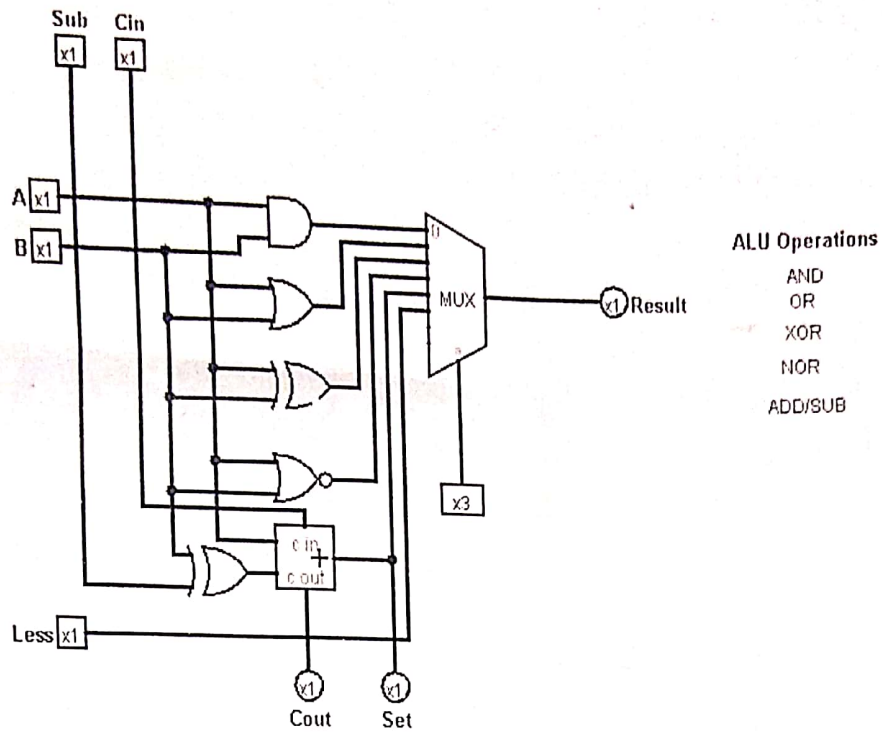


1-bit ALU

 

ALU object

Snapshots

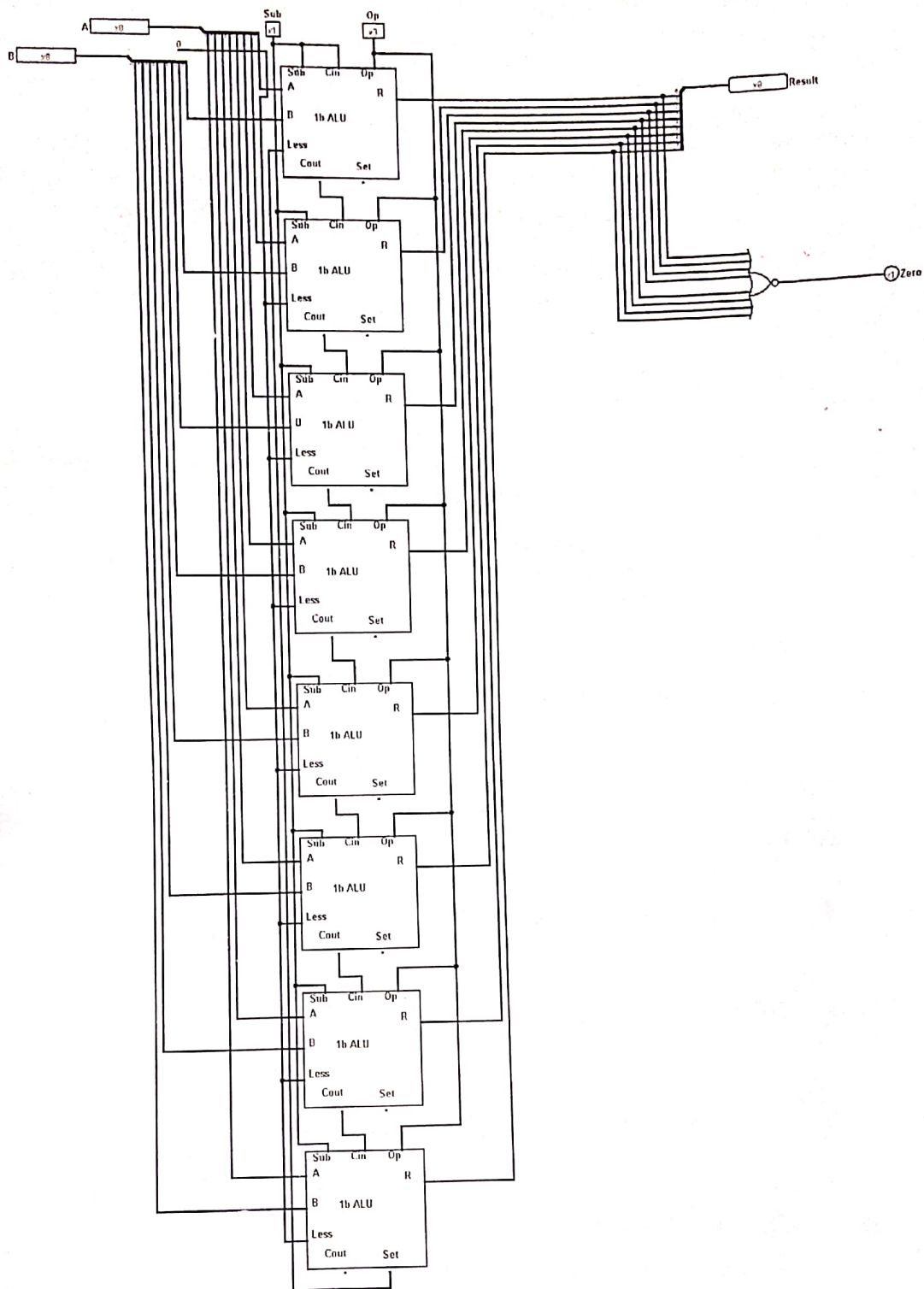

Ramaiah Institute of Technology
(Autonomous Institute, Affiliated to VTU)

Department of CSE

Programme: B.E
Course: Computer Organization

Term: Jan to May 2019
Course Code: CS45

Activity VI: Designing memory system using Logisim simulator.

Name: Muskan Gupta	Marks: /10	Date: 20/5/20
USN: 1MS18CS078	Signature of the Faculty:	

Objective: To simulate the writing operation on memory.

Simulator Description: Logisim is an educational tool for designing and simulating digital logic circuits. With its simple toolbar interface and simulation of circuits as you build them, it is simple enough to facilitate learning the most basic concepts related to logic circuits. With the capacity to build larger circuits from smaller sub circuits, and to draw bundles of wires with a single mouse drag, Logisim can be used (and is used) to design and simulate entire CPUs for educational purposes.



Activity to be performed by students:

List out the steps in designing memory system

1. Add a RAM with separate load and store selected.
 2. Add a counter and connect 0 to A of the RAM.
 3. Add a controller buffer and connect its o/p to RAM.
 4. Add a clock and connect to the i/p of the buffer.
 5. Add a TTY unit with 32 rows and columns.
- Make the connections with RAM.
6. Add a 7-bit random number generator, connect 0 to D.
 7. Add another controlled buffer connect it to TTY. Also add an i/p pin to the buffer.
 8. Connect the o/p of the second buffer to the counter.
 9. Connect a button to the counter.

Observations and Snapshots:

Snapshots -

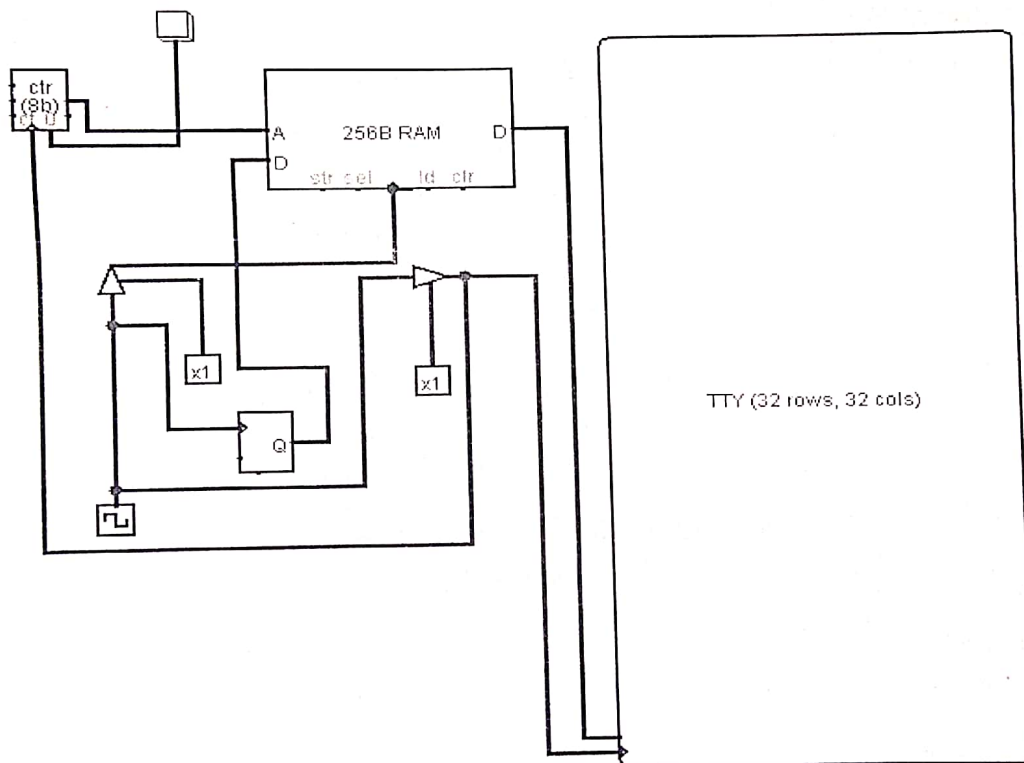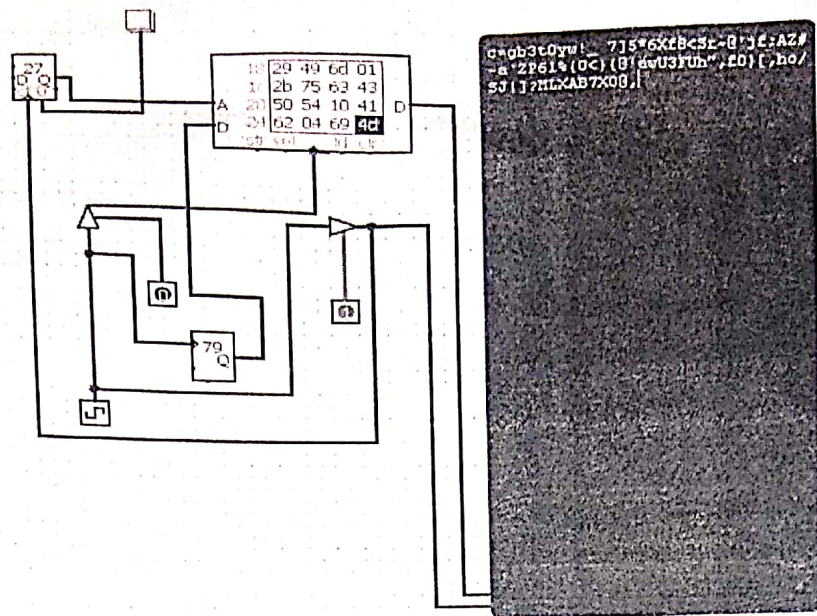

Ramaiah Institute of Technology
(Autonomous Institute, Affiliated to VTU)

Department of CSE

Programme: B.E
Course: Computer Organization

Term: Jan to May 2019
Course Code: CS45

Activity VII: To simulate advantages of using pipeline technique in executing a program.

Name: <u>Muskan Gupta</u>	Marks: <u>/10</u>	Date: <u>22/5/20</u>
USN: <u>IMS18CS078</u>	Signature of the Faculty:	

Objective: To learn and analyze the performance of the CPU by overlapping of instructions using CPUOS-SIM simulator.

Simulator Used: CPUOS-SIM is a software development environment for the simulation of simple computers. It was developed by Dale Skrien to help users to understand computer architectures.

Modern CPU's contain several semi-independent circuits involved in decoding and executing each machine instruction. Separate circuit elements perform each of these typical steps:


- Fetch the next instruction from memory into an internal CPU register.
- Decode the instruction to determine which function sub-circuits it requires.
- Read any input operands required from high-speed registers or directly from memory.
- Execute the operation using the selected sub-circuits.
- Write any output results to high-speed registers or directly to memory.

Separate sections of the CPU circuitry are used for each of these steps. This allows these circuit sections to be arranged into a sequential pipeline, with the output of one step feeding into the next step.

Activity to be performed by students:

With diagram demonstrate the execution of the following instructions using pipelining technique.

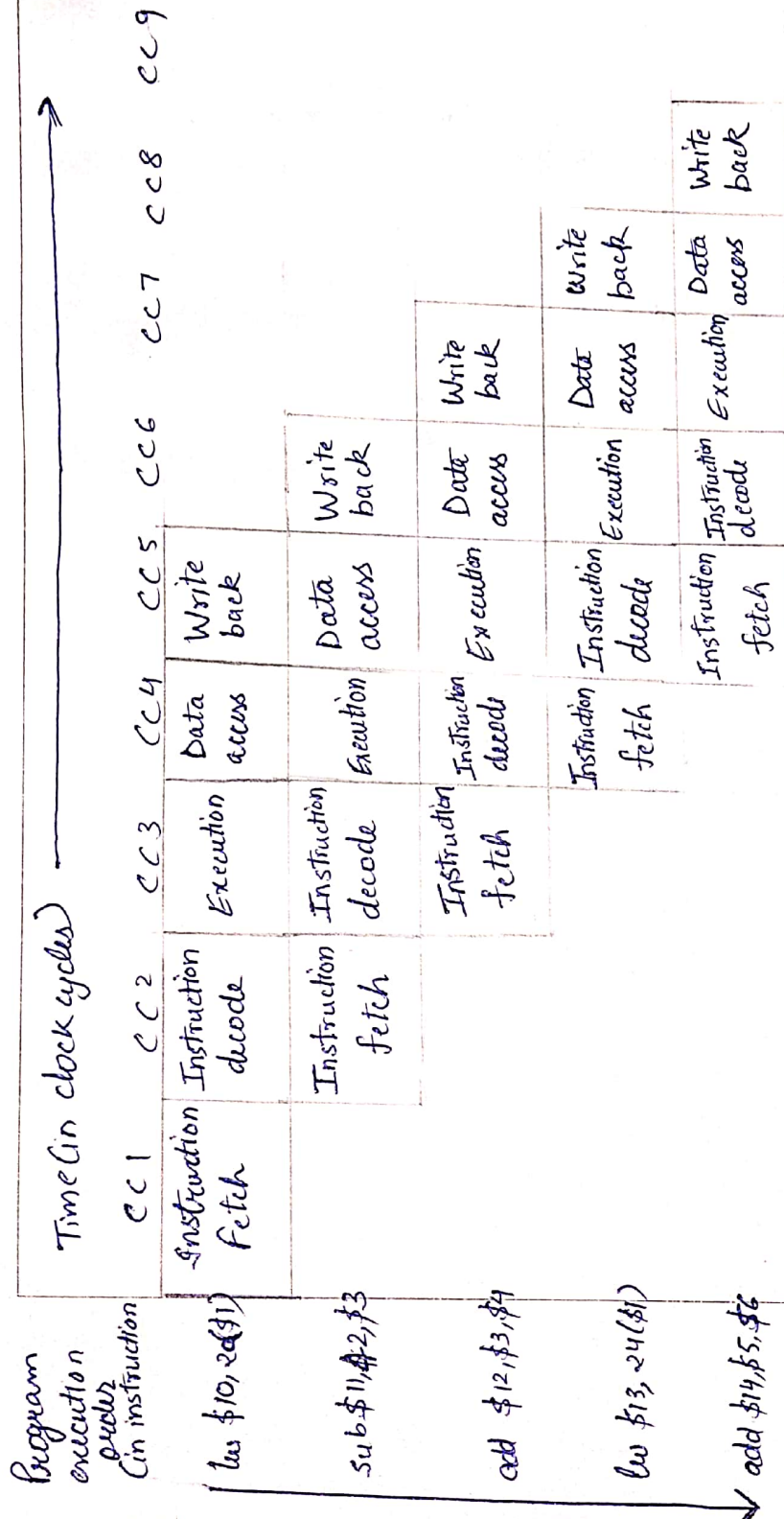lw \$10, 20(\$1)
sub \$11, \$2, \$3
add \$12, \$3, \$4
lw \$13, 24(\$1)
add \$14, \$5, \$6



Time (in clock cycles) →

Program execution order

Instruction
lw \$10, 20(\$1)


sub \$11, 42, \$3

add \$R, \$3, \$4

lw \$13, 24(\$1)

vadd \$14, \$5, \$6

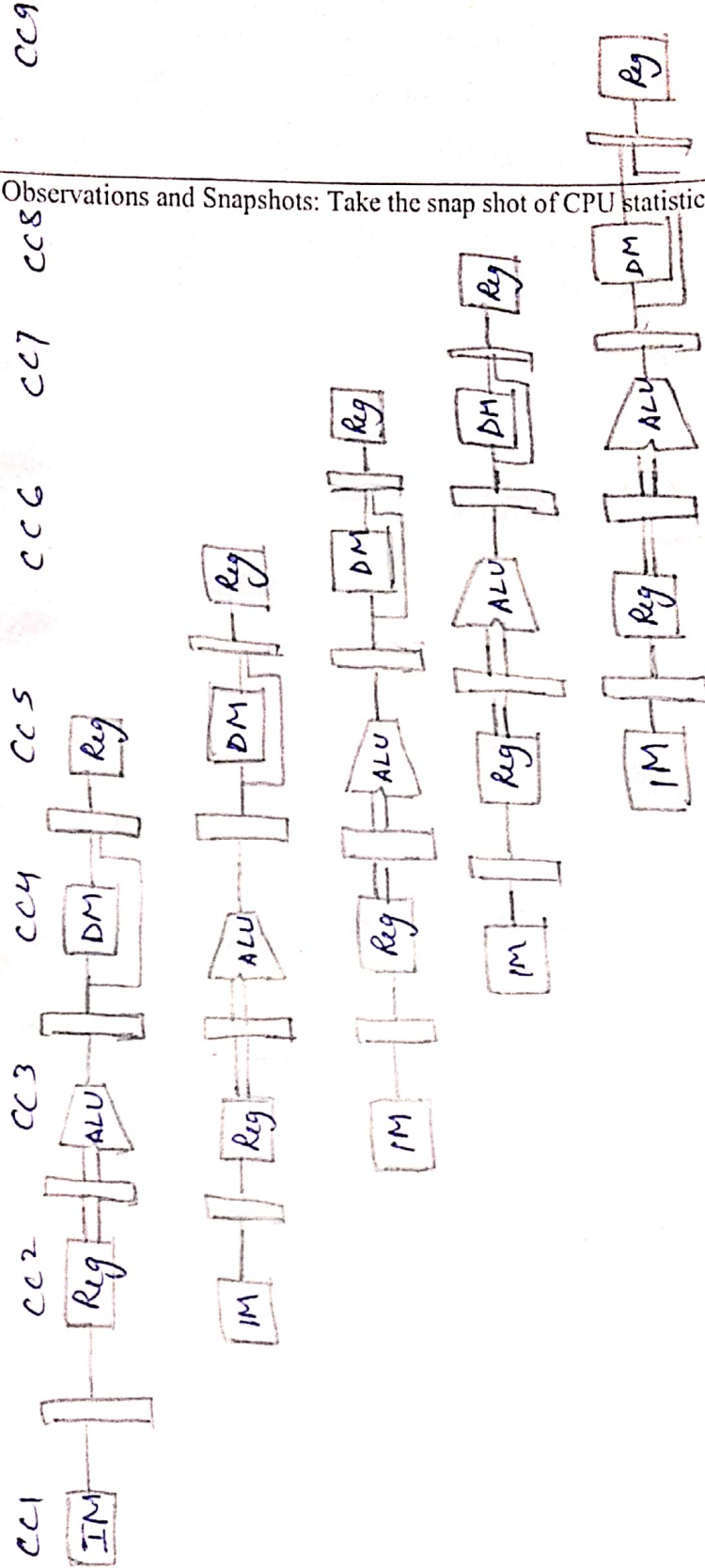Observations and Snapshots: Take the snap shot of CPU statistics and pipeline design.



Snapshots

The screenshot displays a CPU simulator interface with the following components:

- CPU INSTRUCTIONS IN MEMORY (RAM):** A table listing instructions at various memory addresses.

PAddr	LAddr	Instruction	Base	I
1000	0000	LDW @R06, R10	1000	0
1003	0005	SUB #42, R03	1000	1
1011	0011	MOV R03, R11	1000	0
1016	0016	ADD R03, R04	1000	1
1021	0021	MOV R04, R12	1000	0
1026	0026	LDW @R07, R13	1000	0
1032	0031	ADD R05, R06	1000	1
1036	0036	MOV R06, R14	1000	0
1041	0041	HLT	1000	2
- Code-Pipeline:** A section showing the execution of instructions through pipeline stages.
 - Instruction Pipeline:** A list of instructions being processed: SUB #42, R03; MOV R03, R11; ADD R03, R04; MOV R04, R12; LDW @R07, R13; ADD R05, R06; MOV R06, R14; HLT.
 - Pipeline Stages:** A diagram showing the progression of instructions through stages (Fetch, Decode, Read, Execute, Write) over time.
- Statistics:**
 - Clocks: 23
 - Inst. Count: 13
 - CP: 1.77
 - SF: 3.82
 - Busy Stages: 10
 - Data Hazards: 0
 - Control Hazards: 0
 - Inst. Spins: 1
- Colour Code:** A legend for pipeline stages: Fetch (light blue), Decode (light green), Read/Operands (light yellow), Execute (light orange), Write/Result (light red).
- Control:**
 - ☐ Stay on top
 - ☐ No instruction pipeline
 - ☐ Do not insert bubbles
 - ☐ Pipeline stages: 5
 - ☐ No history recording
 - ☒ Enable hazard counts
 - ☐ Stop at instruction LAddr
- History:** A section for navigating through execution history with buttons like 'Fast', 'Slow', 'Load', and 'Save Image'.
- Optimizations:**
 - ☐ Enable operand forwarding
 - ☐ Enable write-back
 - ☐ Support bypass
- GENERAL PURPOSE CPU REGISTERS:** A table showing the current values of registers R00 through R15.

Reg	Val (D)	C	Val (D)
R00	0		
R01	0		
R02	0		
R03	-42		
R04	150		
R05	0		
R06	0		
R07	0		
R08	0		
R09	0		
R10	0		
R11	0		
R12	0		
R13	0		
R14	0		
R15	0		
- Program Stack / Watch:** A section for monitoring the program stack and setting watchpoints.
- Buttons:** Various control buttons including 'ADD NEW', 'SHOW', 'UNDO', 'INSERT ABOVE', 'MOVE DOWN', 'EDIT', 'INSERT BELOW', 'MOVE UP', 'DELETE', 'COPY', 'PASTE ABOVE', 'PASTE BELOW', 'FLUSH', 'SAVE IMAGE', 'SHOW PCB', 'INTERRUPTS', 'CHANGE', and 'RESET ALL'.

Snapshots: